

Seat No.: \_\_\_\_\_

Enrolment No. \_\_\_\_\_

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**MCA - SEMESTER-I • EXAMINATION – WINTER - 2017**

**Subject Code: 3610004**

**Date: 05-01-2018**

**Subject Name: Fundamental of Computer Organization**

**Time: 10:30 am to 01:00 pm**

**Total Marks: 70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)**
- i) What is a BCD code? What are its advantages and disadvantages? **03**
  - ii) Where does complements are used? Compare 1's complement with 2's complement. **03**
  - iii) How many different binary numbers can be stored in a register consisting of six switches ? **01**
- (b)**
- i) Convert 0.4375 decimal number to equivalent binary number. **01**
  - ii) Convert 111011.1011 binary number to equivalent decimal number. **01**
  - iii)  $1001.1 + 1011.01$  **01**
  - iv)  $11.11 - 10.111$  using 2's complement method **01**
  - v)  $1010 * 101$  **01**
  - vi)  $24.1 - 13.4$  using 9's complement method. **01**
  - vii) What is mean by two-state device? **01**
- Q.2 (a)** Simplify the following expressions and draw block diagram of the circuit for each simplified expression, using AND and OR gate. **07**
- i)  $AB'C' + A'B'C' + A'BC' + A'B'C$
  - ii)  $A(A+B+C)(A'+B+C)(A+B'+C)(A+B+C')$
- (b)** Explain the block diagram of basic components of digital computer. **07**
- OR**
- (b)** Write note on magnetic disk memories. **07**
- Q.3 (a)**  $(X, Y, Z, W) = \sum m(4, 6, 7, 8) + D(2, 5, 11, 12)$  using K-map **07**
- 1. Find SOP expression
  - 2. Implement this simplified expression using two level AND-to-OR gate networks.
- Implement this expression using NAND gates only.
- (b)** What do you mean by Addressing Techniques? Explain Indirect and Indexed Addressing techniques with an example **07**
- OR**
- Q.3 (a)** Derive the Boolean algebra expression for gating network that will have output 0 only when  $X=1, Y=1, Z=1$ ;  $X=0, Y=0, Z=0$ ;  $X=1, Y=0, Z=0$ . The output is to be 1 for all other cases. **07**
- 1. Find POS expression
  - 2. Implement this simplified expression using two level OR-to-AND gate network.
- Implement this expression using NOR gates only.
- (b)** Explain the Concepts of Address Bus, Data Bus and Control Bus, Bus Width. **07**
- Q.4 (a)** Explain shift register with wave form and circuit diagram. **07**
- (b)**
- i) Explain full adder using two half adder. **04**

ii) Explain integer representation of binary in digital machines. **03**

**OR**

**Q.4 (a)** Design and explain binary counter to count from 0 to 7. **07**

**(b)** Write working and application of multiplexer. **07**

**Q.5 (a)** Explain various parts of EU in 8086. **07**

**(b)** How to write assembly code for the instruction  $C=A+B$  using zero, one and two addressing technique. **07**

**OR**

**Q.5 (a)** Draw the block diagram of 8086 and explain queue and segment registers. **07**

**(b) i)** Draw the truth table of AND and XOR gate. **03**

**ii)** State De Morgan's theorems. Explain any one **04**

\*\*\*\*\*